


Year 11 Physics
Current Electricity Assignment

1.

- a) $E = F / q = 12 / 8.3 \times 10^{-18} = 1.4 \times 10^{18} \text{ NC}^{-1}$ north /3
 b) $\Delta V = Ed = 1.4 \times 10^{18} \times 1.2 = 1.7 \times 10^{18} \text{ V}$ /2

2. A capacitor stores charge. It has two thin plates on which charges build up. These can be released quickly from here when needed later. /2

3.

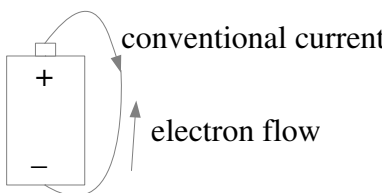
- a)  /2


- b) Heat, Length of wire, Thickness of wire, Material the wire is made of /2


4.

- a) 1 amp = 1 C/s so 12 coulombs every second. $12 \times 5 = 60$, so 60 coulombs flow every second. 1 coulomb = 6.24×10^{18} electrons, so $60 \times 6.24 \times 10^{18} = 4 \times 10^{20}$ electrons flow in five seconds (1 s.f.) /2
 b) $W = Vq = 10\text{J}$ (1 s.f.) /2
 c) $P = VI = 20\text{W}$ (1 s.f.) /2
 d) $Ah = A \times h$, so $h = Ah / A = 2.5 / 3.125 \times 10^{-1} = 8.000$ hours (4 s.f.) /3

5. Consider the following circuits and determine the total resistance in each circuit.

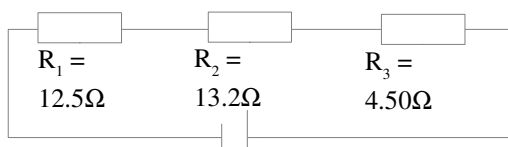- a)  $R_T = R_1 + R_2 + R_3 = 30.2\Omega$ (3 s.f.) /2

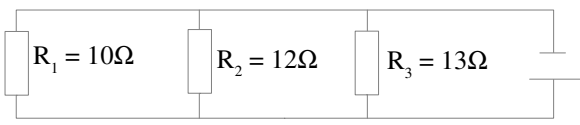- b)  $R_T = 1 / (1/R_1 + 1/R_2 + 1/R_3) = 3.8\Omega$

- c)  /2
 $R = V / I = 25 / 2 = 10\Omega$ (1 s.f.) /2

TOTAL /24